

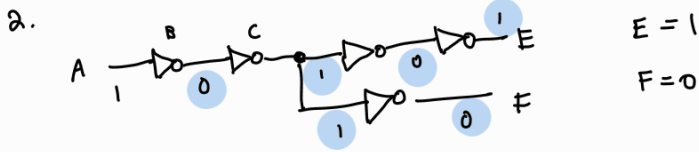


3-1

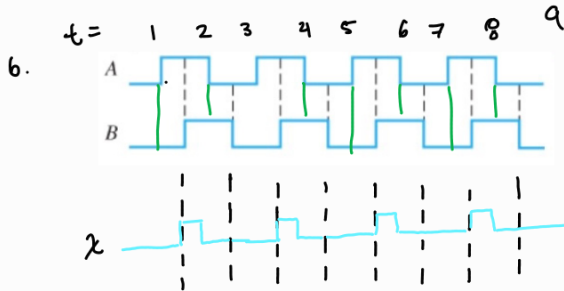


3-2

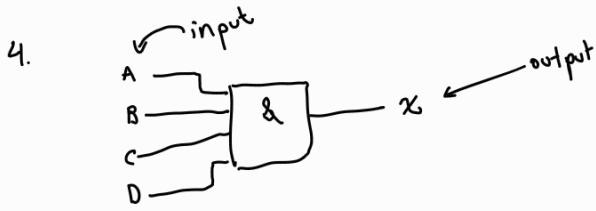

A	B	X
0	0	0
1	0	0
0	1	0
1	1	1

3-3



12. Repeat #7 for a 3 input OR

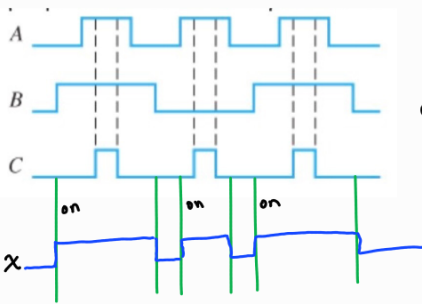

\therefore At least one input must be on

3-4


18.

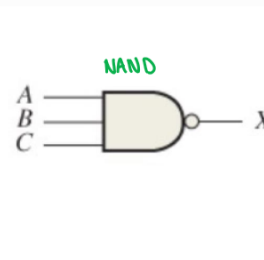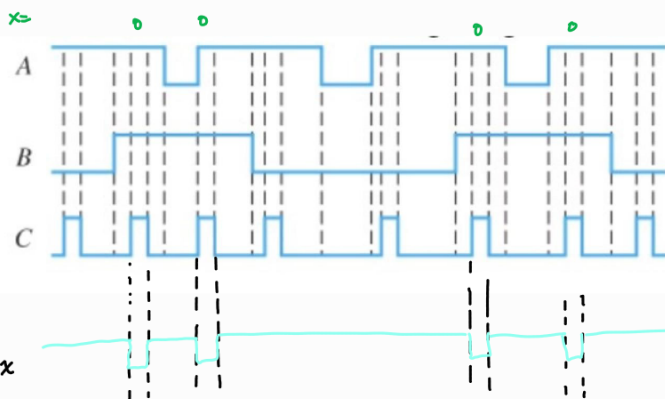

\therefore output = 0 when all inputs are on



3-5

22.

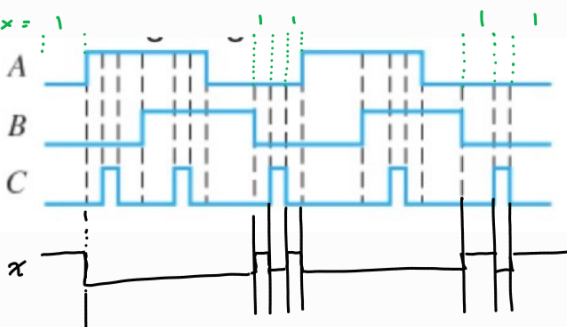

\therefore inputs A, B, C must = 0 for $X = 1$

3-6 2b. #17 For XOR gate

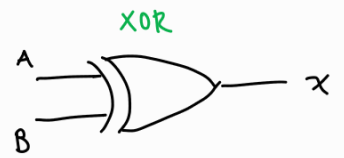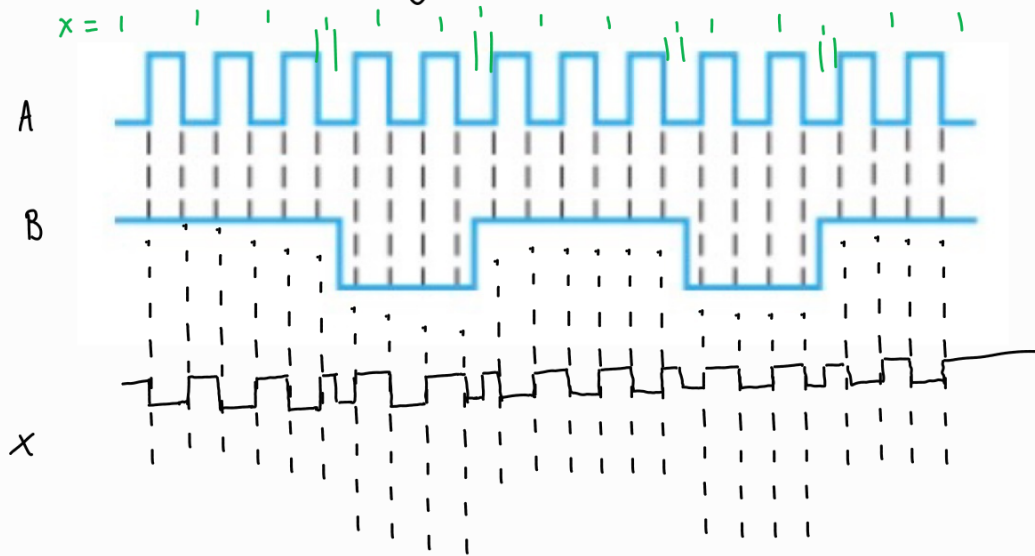

\therefore when A or B is exclusively on $x = 1$

3-8

3b.

Gate A = $t_{PLH} = t_{PLH} = 6\text{ns}$

\swarrow 6 ns

Gate B = $t_{PLH} = t_{PLH} = 10\text{ns}$